

# Experiment 3

## Introduction to Voltage, Current, and Resistance Measurements

Ahmet Akman 2442366  
Assistant : Aybora Köksal

November 16, 2021

### 1 Introduction

In this experiment, as students, we are expected to experiment with how to use measure voltage, current, and resistance by completing the steps described in the third experiment laboratory manual. Throughout these steps, how to determine the resistance via reading resistor color codes and using a multimeter is expected to be learned. As students, we are expected to discriminate the analog and digital multimeters by considering their internal voltage sources. It is observed how to measure the AC line voltage. How to measure DC current and voltage, how the potentiometer works, the characteristics of linear and non-linear resistors, and equivalent resistances are observed by connecting the multimeters directly to each other and the circuit. The results of the steps were noted and plotted for further comments.

### 2 Experimental Results

In this section, the results of Experiment 3 are discussed.

#### 2.1 Step 1

In this step, the resistances of the three resistors are read and measured.

##### 2.1.1 a

The resistances of the resistors are noted after reading them using the color code convention. In Table 1, the values are given.

Table 1: Resistance reading by color code convention.

Color Order	Value	Tolerance
Brown / Black / Red / Gold	1k $\Omega$	% 5
Yellow / Violet / Red / Gold	4.7k $\Omega$	% 5
Brown / Grey / Orange / Gold	18k $\Omega$	% 5

### 2.1.2 b

The resistances of the resistors are measured using a digital multimeter. The measurements are given in Table 2.

Table 2: Resistance reading by color code convention.

Resistor	Measured Value
1k $\Omega$	0.987k $\Omega$
4.7k $\Omega$	4.865K $\Omega$
18k $\Omega$	17.851k $\Omega$

It is observed that the actual value of the resistances can be different from their expected value. This difference could be stemmed from environmental factors as well as probing. Although there is a precision factor, the tolerance values are verified.

## 2.2 Step 2

In Step 2, the digital multimeter instrument is used only. Using the resistance measurement feature of the multimeter, the resistance value of the opposing ends of the 1K and 10K potentiometers are measured. Then The maximum and minimum resistance values between their middle terminals and other terminals are recorded. The recorded resistance values are provided in Table 3.

Table 3: Resistance measurements of the potentiometer

Potentiometer	Resistance Between Opposing Ends	Maximum Resistance	Minimum Resistance
1k $\Omega$	0.983k $\Omega$	0.981k $\Omega$	0.001 $\Omega$
10k $\Omega$	8.695k $\Omega$	8.690k $\Omega$	0.004 $\Omega$

It can be inferred that the resistance does not change when we connect the measurement probes to the opposing ends because there is a static resistance between those terminals which approximately corresponds to the maximum value of the dynamic terminal.

## 2.3 Step 3

In this step, the internal battery voltages of the analog and digital multimeters are measured and compared.

### 2.3.1 a

Analog multimeter is set for resistance measurement. Then the digital multimeter is set to voltage measurement, and its probes are connected to the probes of the analog multimeter. As a result, even though the ohmmeter scale is different, the measured voltage is observed as constant. The measurements are given in Table 4.

Table 4: Internal battery measurements of the analog multimeter.

Scale	Voltage Value
x1 $\Omega$	-1.5924 V
x10 $\Omega$	-1.5924 V
x100 $\Omega$	-1.5921 V
x1k $\Omega$	-1.5890 V

### 2.3.2 b

Digital multimeter is set for resistance measurement. Then the analog multimeter is set to voltage measurement, and its probes are connected to the probes of the digital multimeter. So, the internal battery voltage differs when the digital multimeter is set to different ohmmeter scales. The measurements are given in Table 5.

Table 5: Internal battery measurements of the digital multimeter.

Scale	Voltage Value
x100 $\Omega$	6V
x1k $\Omega$	6V
x10k $\Omega$	6.25 V
x100k $\Omega$	3V
x1M $\Omega$	1.5V
x10M $\Omega$	$\sim 0.1$ V (or zero)
x100M $\Omega$	$\sim 0.1$ V (or zero)

This result shows us that digital multimeters are able to adjust their internal voltage when they are measuring resistances in different scales. It can be concluded that digital multimeters have higher precision in measurement.

## 2.4 Step 4

In this step, the line voltage is measured using analog multimeter. Multimeters range is set "500V AC". The measurement is stated in Table 6.

Table 6: Line voltage measurement

Line Voltage	Approximately $220V_{ac}$
--------------	---------------------------

## 2.5 Step 5

In Step 5, power supply and digital multimeter instruments are used. The circuit in Figure 1 is constructed on the breadboard.

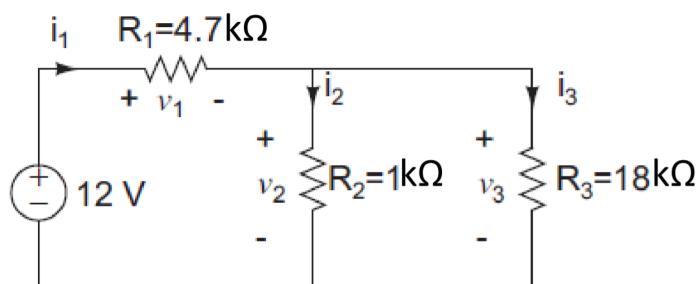


Figure 1: Circuit schematic for the step 5

Then the required voltage and current measurements are made. The measurements are given in Table 7.

Table 7: Voltage and current measurements for the step 5

$V_1$	$V_2$	$V_3$
10.041V	1.948V	1.948
$i_1$	$i_2$	$i_3$
2.064mA	1.957mA	0.109mA

## 2.6 Step 6

In this step, power supply, analog multimeter, and digital multimeter instruments are used. The circuit illustrated in Figure 2 is set.

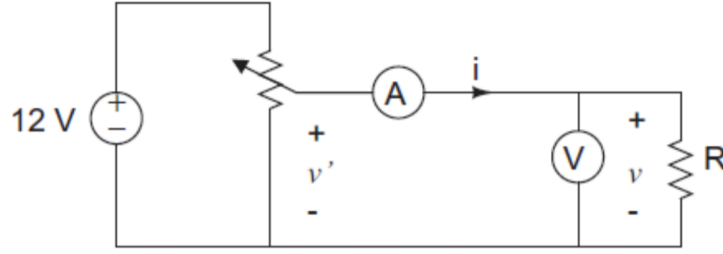


Figure 2: Circuit schematic for the step 6

The resistor with resistance "R" is selected as "4.7k $\Omega$ ". The potentiometer is adjusted so that the voltage value becomes 9, 7, 5, 0 volts. For all cases, the current  $i$  is measured and recorded.

### 2.6.1 a

The current and voltage measurements are made and plotted in MATLAB. The Figure 3 shows  $i$  versus  $v$ . The resistor with resistance "R" is measured as approximately "4.602k $\Omega$ " using the equation "  $R = \frac{V}{I}$  ".

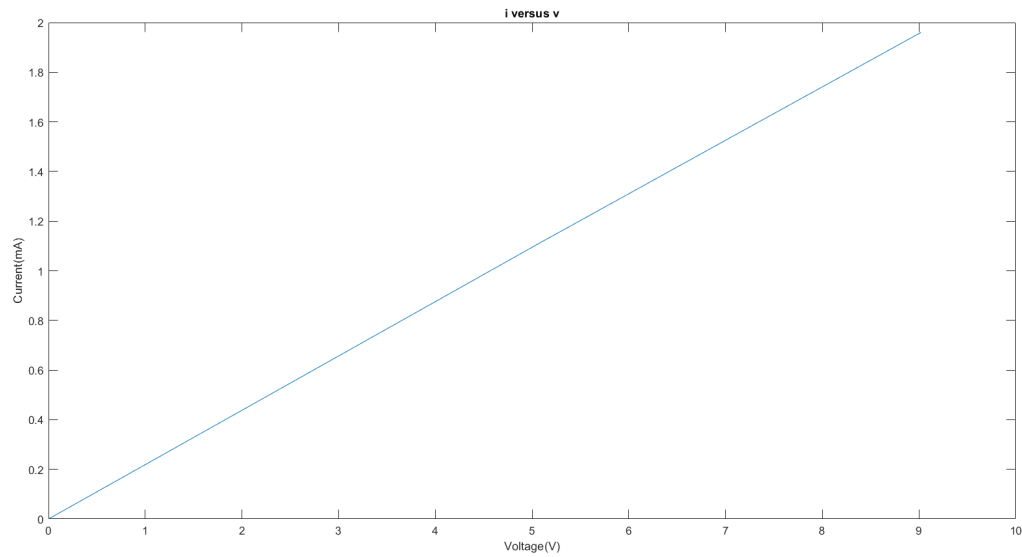


Figure 3: Plot of  $i$  versus  $v$

### 2.6.2 b

The resistor with resistance "R" is measured as approximately "4k $\Omega$ " using analog multi-meter.

### 2.6.3 c

The resistor with resistance "R" is measured as "4.60k $\Omega$ " using digital multimeter.

### 2.6.4 d

It can be seen from Figure 3 that the plot is approximately linear. This is because the equation of  $R$  (*constant*) =  $\frac{V}{I}$ . Also, the measurements from the analog and digital multimeters practically show that the digital multimeters have higher resolution, whose measurement is approximately the same as the experimental and given resistance data.

## 2.7 Step 7

In step 7, the circuit given in Figure 3 is set up. The analog multimeter is set as a voltmeter, and the digital multimeter is set as an amperemeter.

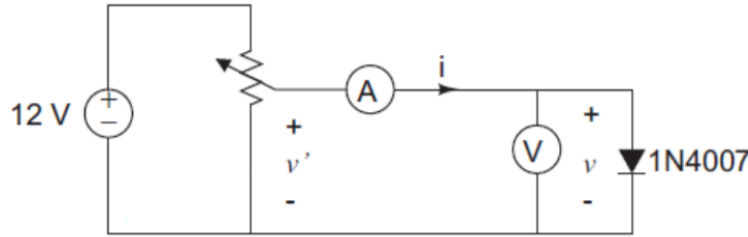


Figure 4: Circuit schematic for the step 7

After all the connections are made, 100k $\Omega$  pot is used for the first three measurements. The 10k $\Omega$  pot is used for the following two measurements, and the 1k $\Omega$  is used for the last two measurements. This procedure is done by different potentiometers in order not to burn the circuit. The measurements are given in Table 8. The measurements are made by adjusting the pot slowly with respect to amperemeter readings.

Table 8: The data collected from the multimeters

Current measured by amperemeter	Voltage measured by voltmeter.
200 $\mu$ A	0.45 V
500 $\mu$ A	0.48 V
1mA	0.55 V
2mA	0.6 V
5mA	0.65 V
10mA	0.61 V
20mA	0.7 V

The plot of  $i$  versus  $v$  is given in the Figure 4.

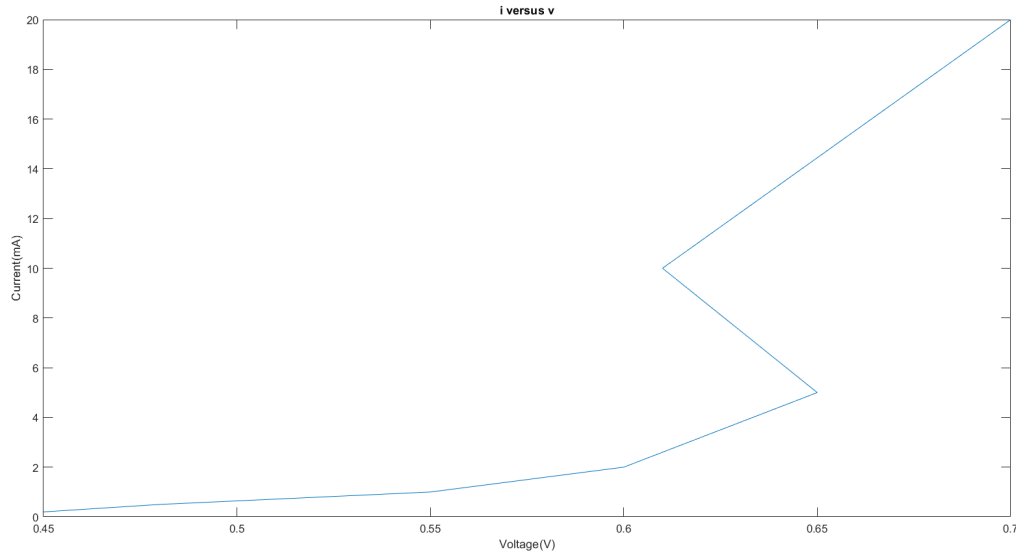


Figure 5: Plot of  $i$  versus  $v$

It can be inferred that the component called "diode" is not a linear component. The Z shape in the figure might occur due to the analog multimeters' precision loss.

### 3 Conclusion

In conclusion, in experiment 3, "Introduction to Voltage, Current, and Resistance Measurements", as students, we have learned how to use different kinds of multimeters and potentiometers in general. The experiment was conducted in 7 steps. To determine the resistance of an unknown resistor, color code reading and multimeters measurement techniques are used. The resistance values of various potentiometers are obtained across different terminals and commented on. The internal batteries voltages of the analog and digital multimeters are measured, and it concluded that digital multimeters have higher measurement accuracy. The city line AC voltage is measured with analog multimeter. Voltage and current measurements are made on a circuit. The terminal characteristics of linear and non-linear resistors are observed. The properties of a potentiometer are explored on a resistive circuit. Current and voltage measurements are made for the diode on a circuit. The non-linear behavior of the diode component is observed in the data. In this experiment, as students, we have experimented with how to use different kinds of multimeters for measurements and how to work with potentiometer components.

## Appendix I

Total time spent on/during:

- Pre-lab preparation: 1 hours (including the preliminary work and simulations)

- Experimental work: 2 hours (hours spent in lab)
- Report writing: 4.5 hours