

Experiment 4

Resistive Circuits

Ahmet Akman 2442366

Assistant : Şirin Yazar

November 23, 2021

1 Introduction

In this experiment, as students, we are expected to experiment with how to use measure voltage, current, and resistance by completing the steps described in the third experiment laboratory manual. Throughout these steps, how to determine the resistance via reading resistor color codes and using a multimeter is expected to be learned. As students, we are expected to discriminate the analog and digital multimeters by considering their internal voltage sources. It is observed how to measure the AC line voltage. How to measure DC current and voltage, how the potentiometer works, the characteristics of linear and non-linear resistors, and equivalent resistances are observed by connecting the multimeters directly to each other and the circuit. The results of the steps were noted and plotted for further comments.

2 Experimental Results

In this section, the results of Experiment 4 are discussed.

2.1 Step 1

2.1.1 a

In this step, the circuit given in Figure 1 is constructed. The V_{pp} is selected as 12 and the frequency is adjusted as 50 Hz. The channel 2 of the oscilloscope is connected to the terminals of rightmost resistor.

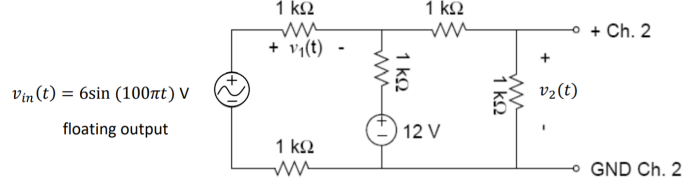


Figure 1: Circuit schematic for the step 1 section *a*

As a result the $V_2(t)$ is observed and plotted. The plotting is given in the Figure 2.

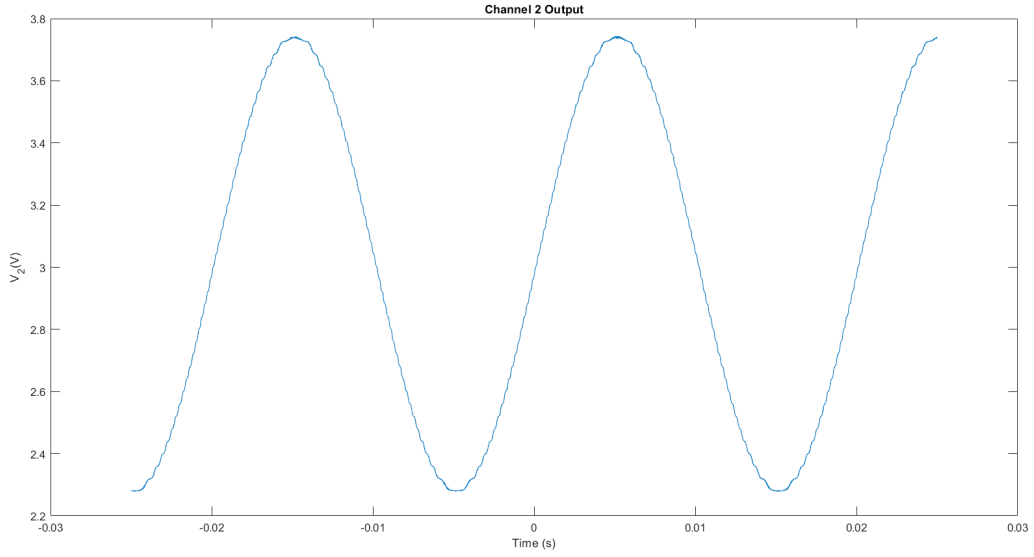


Figure 2: V_2 versus time(s)

2.1.2 b

In this step, the circuit given in in Figure 1 is used. As measurement setup, probes of the channel 1 is connected additionally. The setup is given in Figure 3.

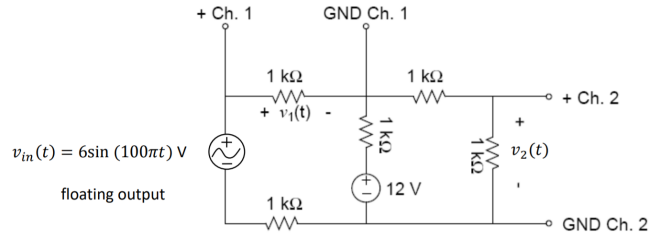


Figure 3: Circuit schematic for the step 1 section *b*

As a result the values of V_1 and V_2 are observed and plotted. The plotting is given in Figure 4.

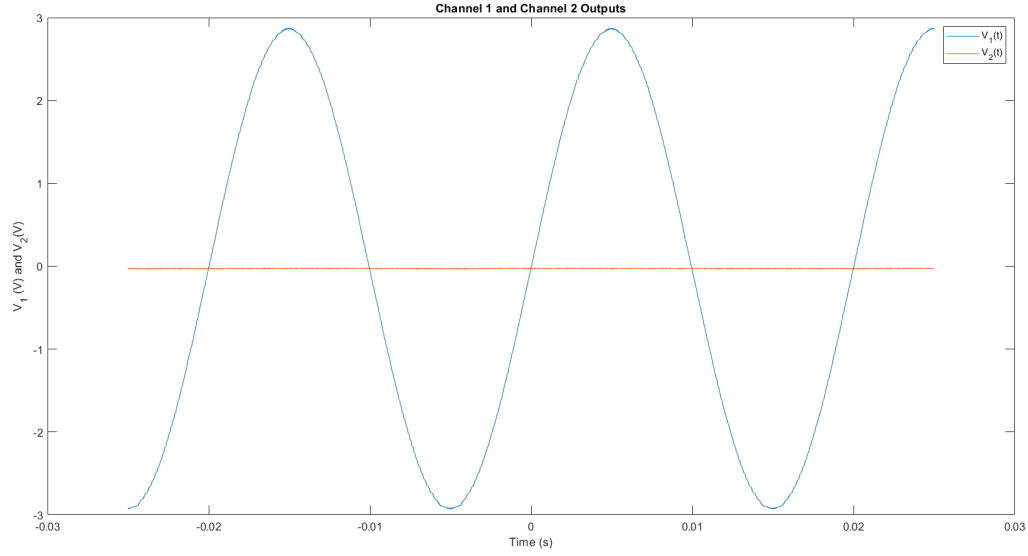


Figure 4: V_1 V_2 versus time(s)

As it can be seen from the plot channel 2 is approximately corresponds to "0" value, although it is not supposed to be so. The measurement probe of the second channel is connected between two ground terminals of the oscilloscope. This result demonstrates that grounding configuration of the oscilloscope may prevent the accurate observations.

For comparison the values measured and calculated theoretically are given in the Table 1.

Table 1: Calculated values and measured values.

X	Calculated (V)	Measured (V)
V_1	$\frac{9}{5} \sin 100\pi t - 3$	1.5275
V_2	$\frac{3}{4} \sin 100\pi t + 3$	7.477

2.2 Step 2

In Step 2, the circuit diagram given in the Figure 5 is constructed in the LTspice environment. Measurement probe nodes are indicated with texts on the figure.

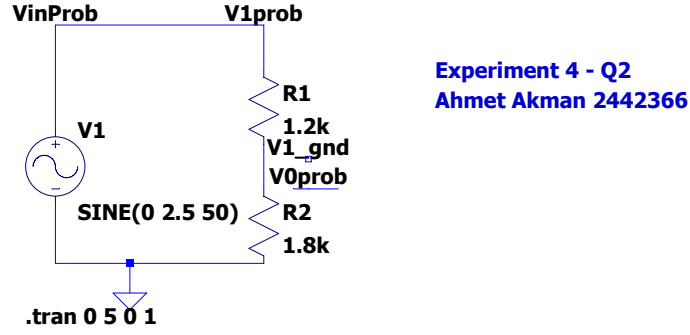


Figure 5: The circuit diagram for the Step 2

2.2.1 a

For the drawn circuit, V_{in} is set as 50 Hz and 5 V_{pp} . As a result the plot given in Figure 6 is obtained.

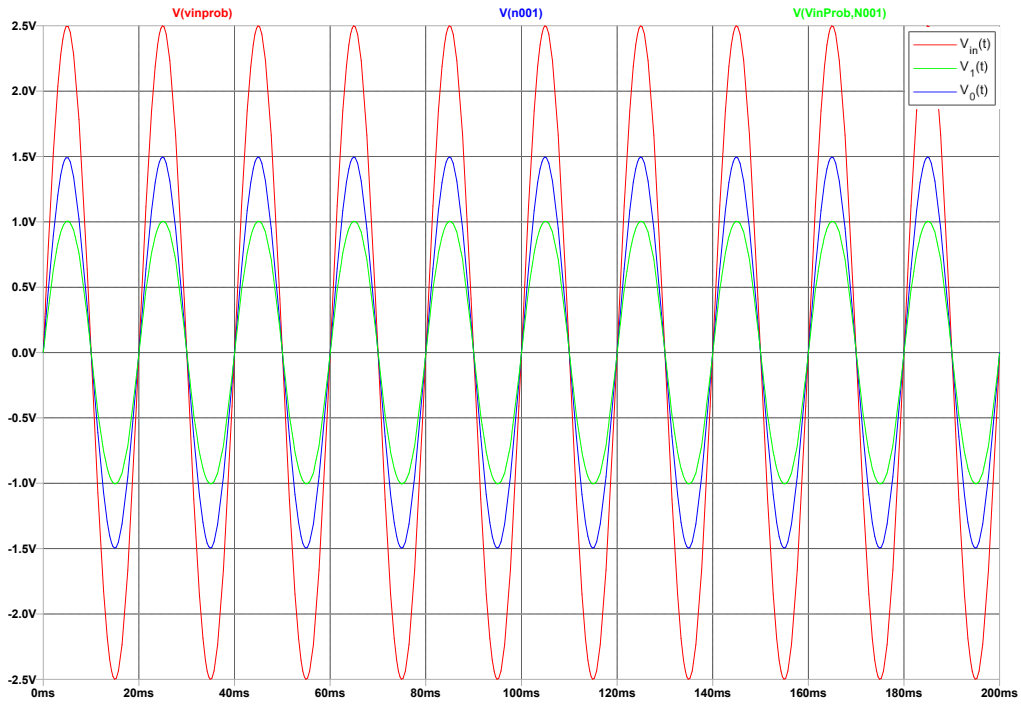


Figure 6: The plot of V_{in} V_0 V_1 versus time(ms)

2.2.2 b

When the V_{in} is displayed only it can be said that V_{pp} is equal to "2" volts which is the same amplitude we found in part a.

2.3 Step 3

In this step, signal generator and oscilloscope instruments are used. The circuit given in the Figure 7 is constructed.

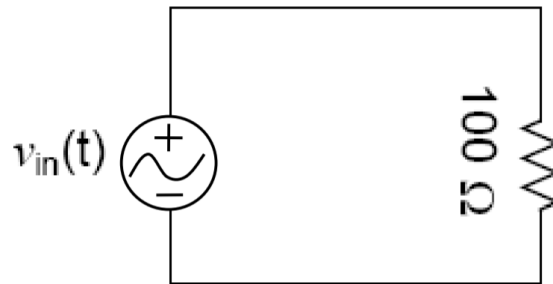


Figure 7: V_{in} versus time (s)

Before connecting the signal generator to the circuit, the terminals are directly connected to the oscilloscope probes. Then the observations are made, and the output is given in the Figure 8. The V_{pp} is measured as 3 volts.

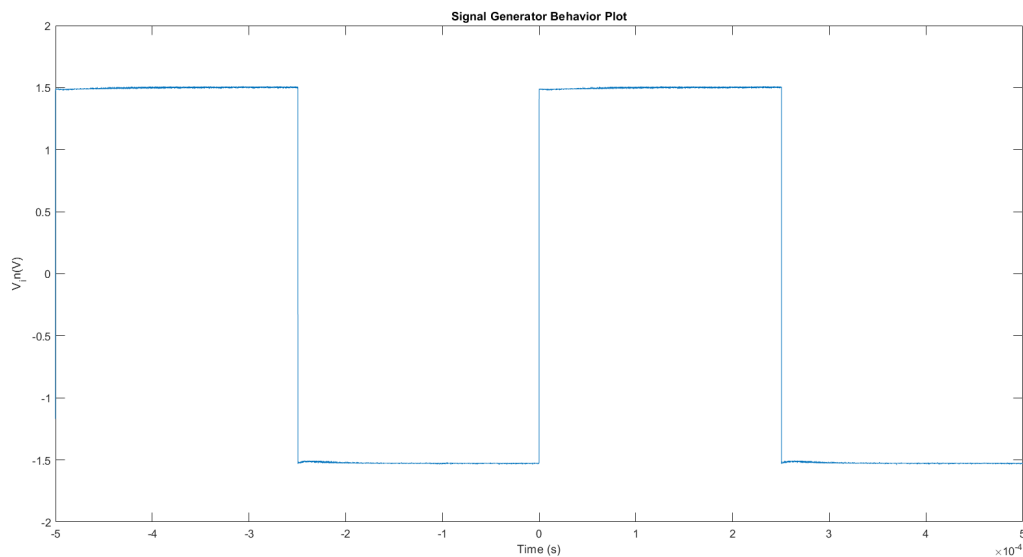


Figure 8: V_{in} versus time (s)

The signal generator is connected to the circuit. The measurements are displayed on the screen of DSO. Then the data plotted are given in the Figure 9.

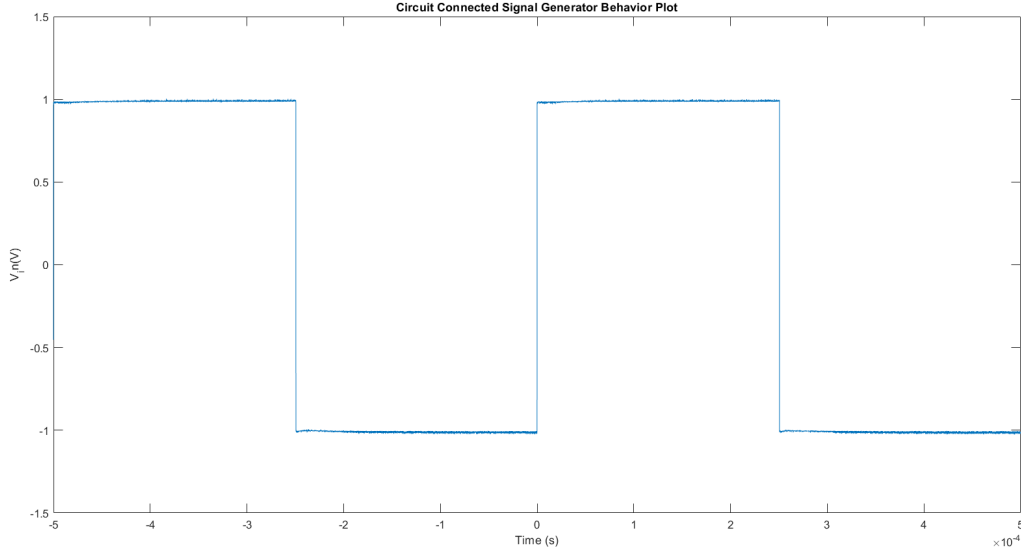


Figure 9: V_{in} versus time (s)

As a result , it can be seen that the drops in the amplitude is stemmed from the non-ideal behavior of the signal generator. It is said that the signal generator has a $50\ \Omega$ internal resistance, so when a comparable resistance is connected the voltage is divided. It can be seen from the Figure 9, amplitude is dropped to 3 volts.

2.4 Step 4

In this step, the circuits given in the Figure 10 are set. And the source voltage is measured as 5 volts.

2.4.1 a

The range of the analog multimeter is set to 5 V DC. The internal resistance of the analog multimeter is measured via digital multimeters resistance mode. The obtained internal resistance is " $99.705\text{k}\Omega$ ". All the voltage measurements are made using analog multimeter.

2.4.2 b

All the measurements are repeated and recorded using digital multimeter. For the comparison, the readings of the analog and digital multimeters are given in the Table 2.

2.5 Step 5

In Step 5, power supply and digital multimeter instruments are used. The circuit in Figure 1 is constructed on the breadboard.

Then the required voltage and current measurements are made. The measurements are given in Table 7.

2.6 Step 6

In this step, power supply, analog multimeter, and digital multimeter instruments are used. The circuit illustrated in Figure 2 is set.

The resistor with resistance "R" is selected as "4.7k Ω ". The potentiometer is adjusted so that the voltage value becomes 9, 7, 5, 0 volts. For all cases, the current i is measured and recorded.

2.6.1 a

The current and voltage measurements are made and plotted in MATLAB. The Figure 3 shows i versus v . The resistor with resistance "R" is measured as approximately "4.602k Ω " using the equation " $R = \frac{V}{I}$ ".

2.6.2 b

The resistor with resistance "R" is measured as approximately "4k Ω " using analog multimeter.

2.6.3 c

The resistor with resistance "R" is measured as "4.60k Ω " using digital multimeter.

2.6.4 d

It can be seen from Figure 3 that the plot is approximately linear. This is because the equation of R (*constant*) = $\frac{V}{I}$. Also, the measurements from the analog and digital multimeters practically show that the digital multimeters have higher resolution, whose measurement is approximately the same as the experimental and given resistance data.

2.7 Step 7

In step 7, the circuit given in Figure 3 is set up. The analog multimeter is set as a voltmeter, and the digital multimeter is set as an amperemeter.

After all the connections are made, 100k Ω pot is used for the first three measurements. The 10k Ω pot is used for the following two measurements, and the 1k Ω is used for the last two measurements. This procedure is done by different potentiometers in order not to burn the circuit. The measurements are given in Table 8. The measurements are made by adjusting the pot slowly with respect to amperemeter readings.

The plot of i versus v is given in the Figure 4.

It can be inferred that the component called "diode" is not a linear component. The Z shape in the figure might occur due to the analog multimeters' precision loss.

3 Conclusion

In conclusion, in experiment 3, "Introduction to Voltage, Current, and Resistance Measurements", as students, we have learned how to use different kinds of multimeters and potentiometers in general. The experiment was conducted in 7 steps. To determine the resistance of an unknown resistor, color code reading and multimeters measurement techniques are used. The resistance values of various potentiometers are obtained across different terminals and commented on. The internal batteries voltages of the analog and digital multimeters are measured, and it concluded that digital multimeters have higher measurement accuracy. The city line AC voltage is measured with analog multimeter. Voltage and current measurements are made on a circuit. The terminal characteristics of linear and non-linear resistors are observed. The properties of a potentiometer are explored on a resistive circuit. Current and voltage measurements are made for the diode on a circuit. The non-linear behavior of the diode component is observed in the data. In this experiment, as students, we have experimented with how to use different kinds of multimeters for measurements and how to work with potentiometer components.

Appendix I

Total time spent on/during:

- Pre-lab preparation: 1 hours (including the preliminary work and simulations)
- Experimental work: 2 hours (hours spent in lab)
- Report writing: 4.5 hours