

Experiment 5 Preliminary Work

Operational Amplifiers

Ahmet Akman 2442366

December 7, 2021

1 Introduction

In preliminary work of the Experiment 5 , the steps for the pre-experiment are conducted and presented.

2 Step 1

Videos in ODTUCLASS related to this experiment is watched and observations are noted.

3 Step 2

"Notes on Op-Amps" documents is studied.

4 Step 3


In this step following 4 op-amp circuits are constructed in the LTSpice environment and simulated. $V_{in(t)}$ is taken as $3\sin(1000\pi)$ Volts. Then data are fetched from LTSpice and plotted in MATLAB.

4.1 a)

Basic comparator circuit is constructed in LTSpice environment. The schematic is given in the Figure 1.



Then plots given in Figures 5,6 and 7 are obtained.

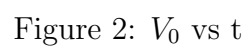

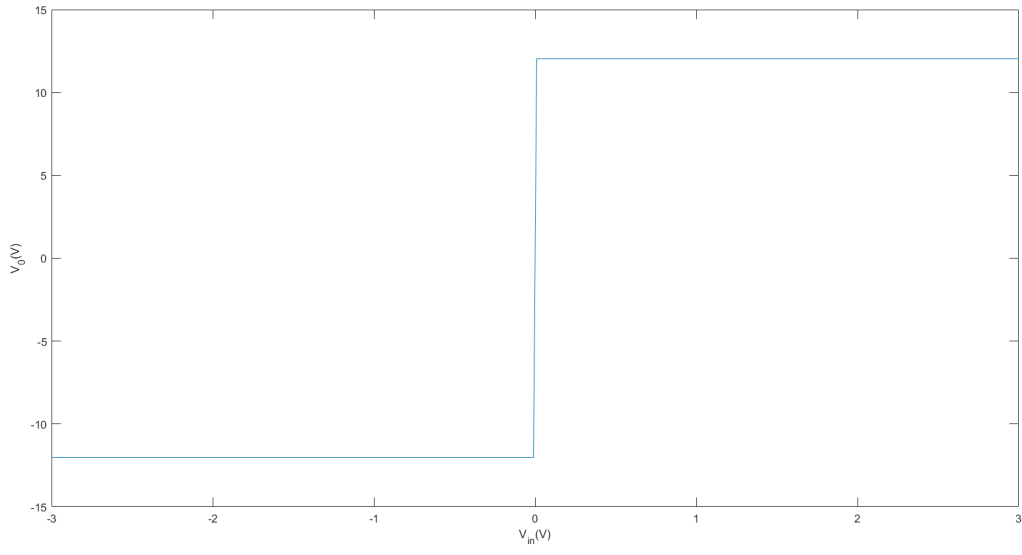


Figure 3: V_0 vs V_{in}

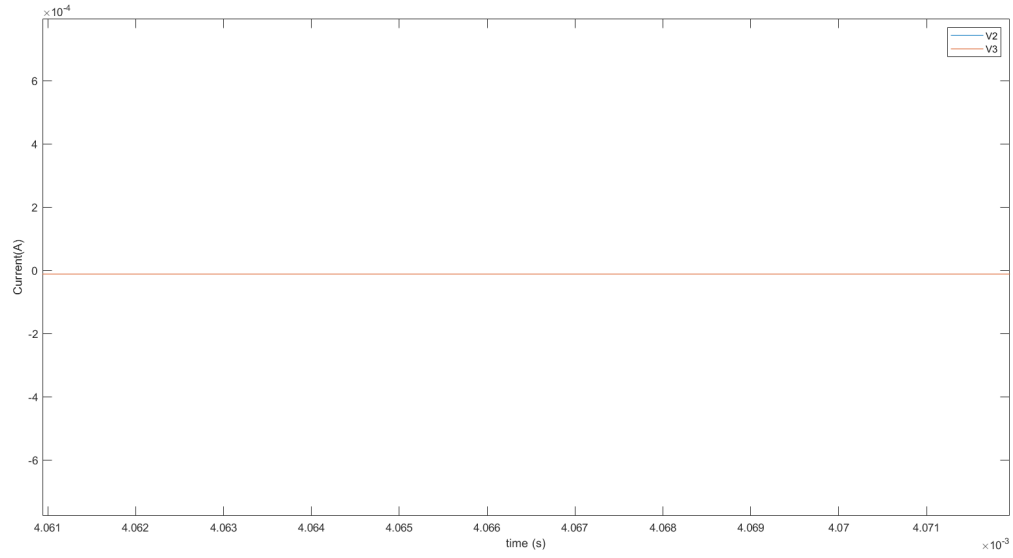



Figure 4: i vs t

4.2 b)

Buffer circuit is constructed in LTSpice environment. The schematic is given in the Figure 8.

Ahmet Akman 2442366

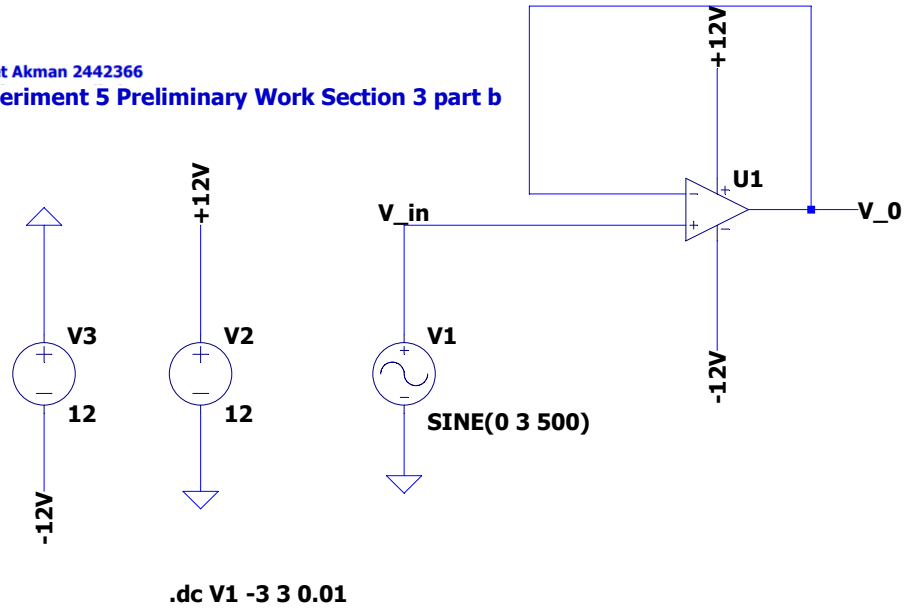Experiment 5 Preliminary Work Section 3 part b



--- C:\akman\METU EEE UNDERGRADUATE EDUCATION\3rdTermFall2021\EE213\EXP5\simulations\Buffer.asc ---

Figure 5: Circuit schematic for the buffer.

Then plots given in Figures 9 , 10 and 11 are obtained.

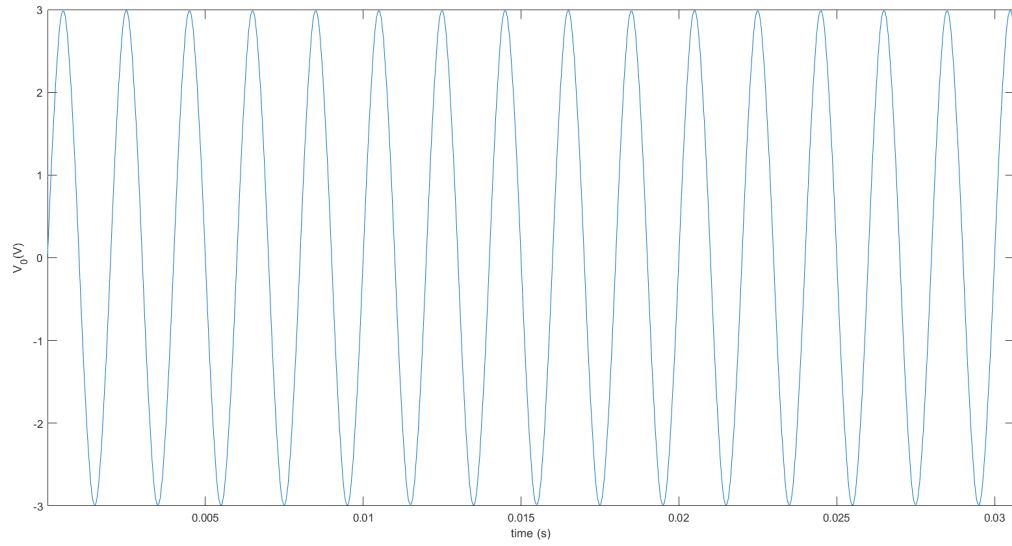


Figure 6: V_0 vs t

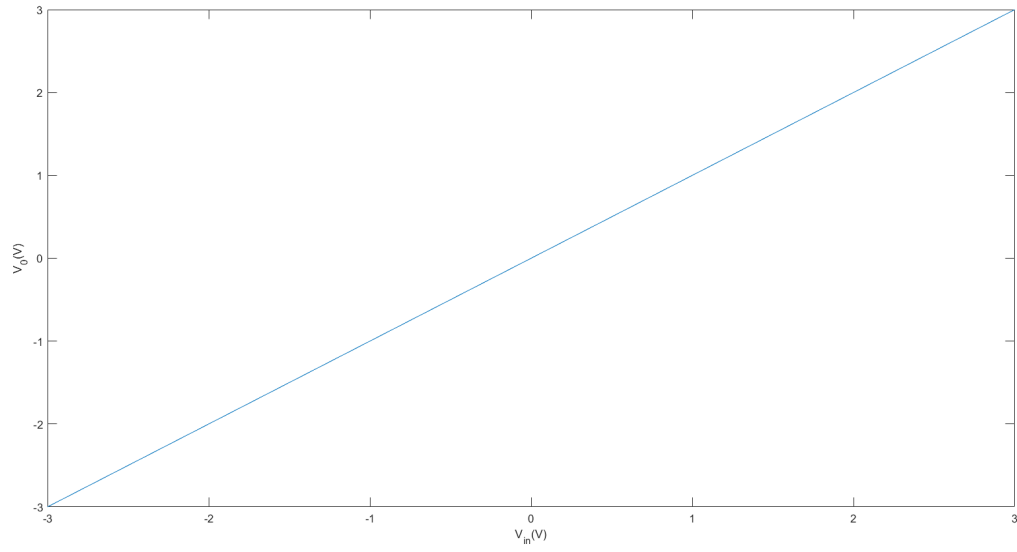


Figure 7: V_o vs V_{in}

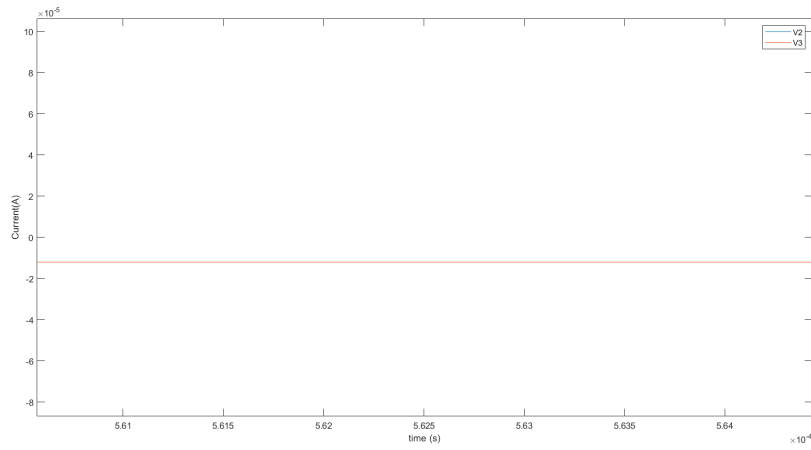



Figure 8: i vs t

4.3 c)

Inverting amplifier circuit is constructed in LTSpice environment. The schematic is given in the Figure 12.

Ahmet Akman 2442366

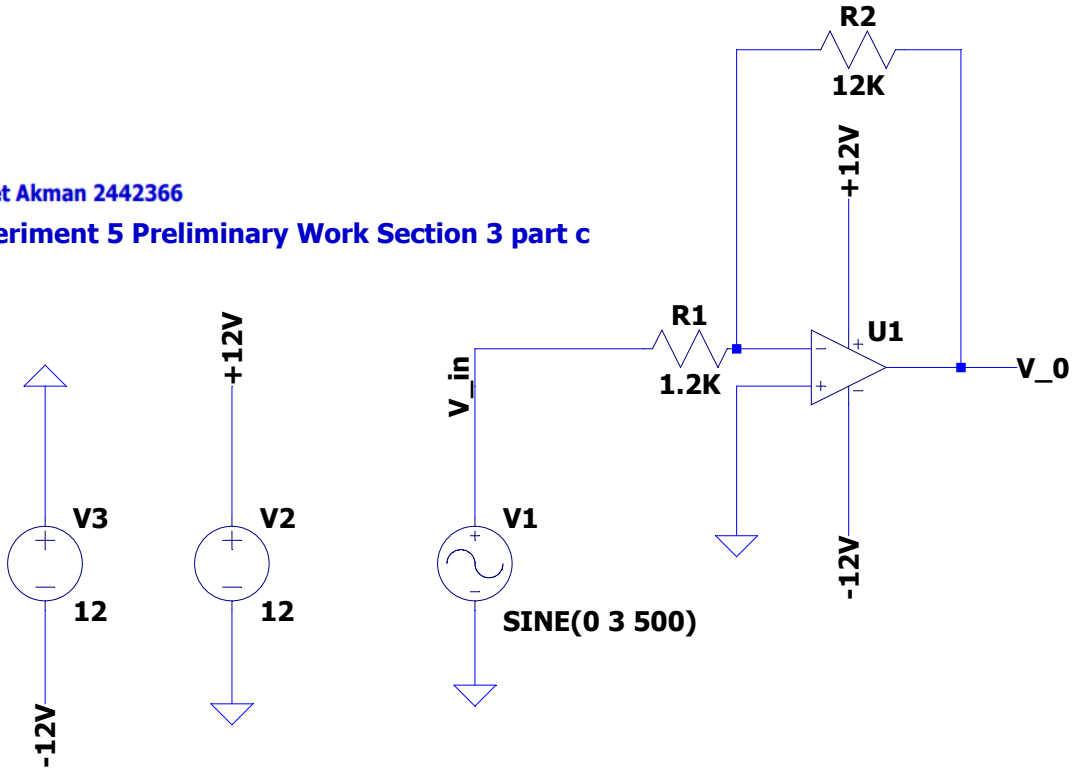Experiment 5 Preliminary Work Section 3 part c



.dc V1 2 0

--- C:\akman\METU EEE UNDERGRADUATE EDUCATION\3rdTermFall2021\EE213\EXP5\simulations\Inverting.asc ---

Figure 9: Circuit schematic for the inverting amplifier.

Then plots given in Figures 13,14 and 15 are obtained.

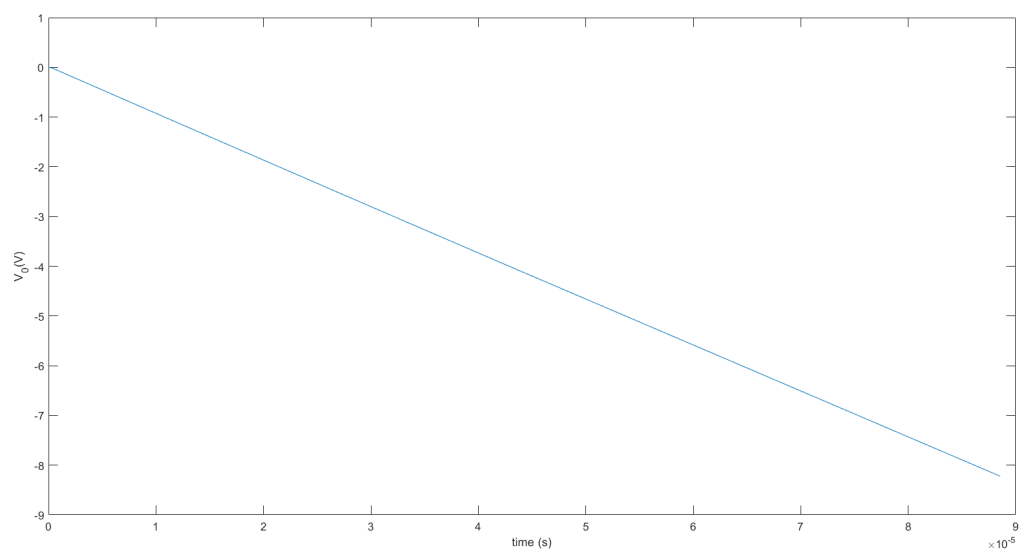


Figure 10: V_0 vs t

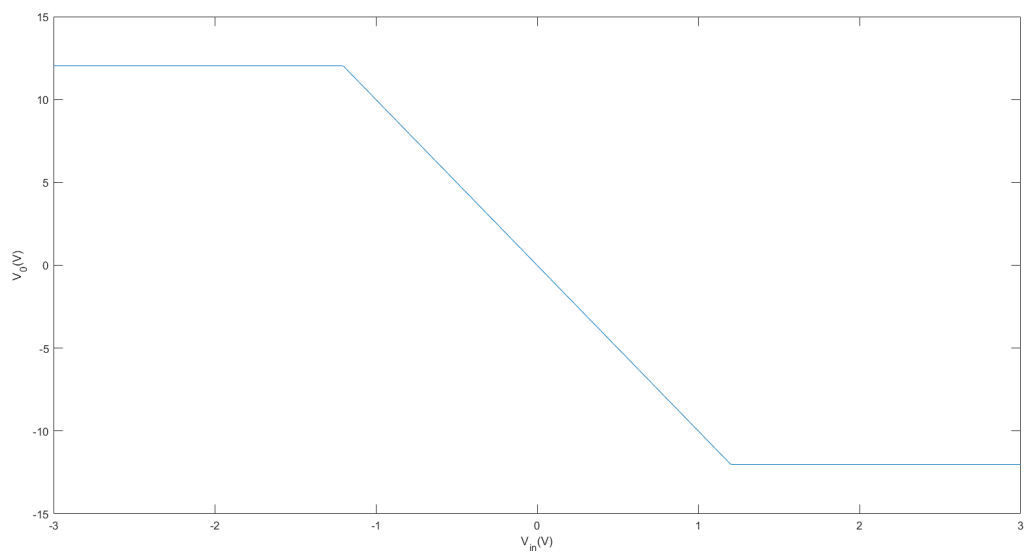


Figure 11: V_0 vs V_{in}

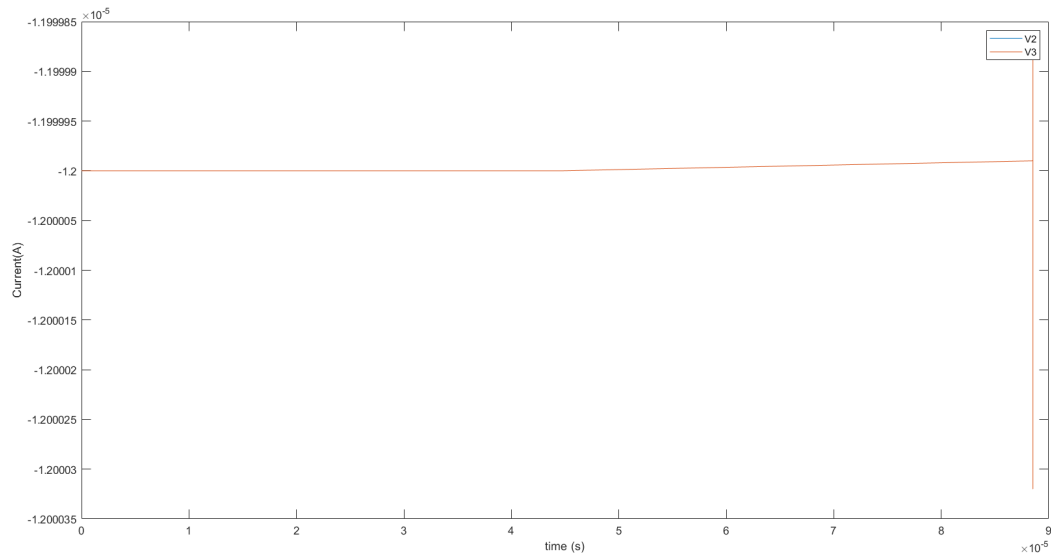


Figure 12: i vs t

4.4 d)

Non-inverting amplifier circuit is constructed in LTSpice environment. The schematic is given in the Figure 16.

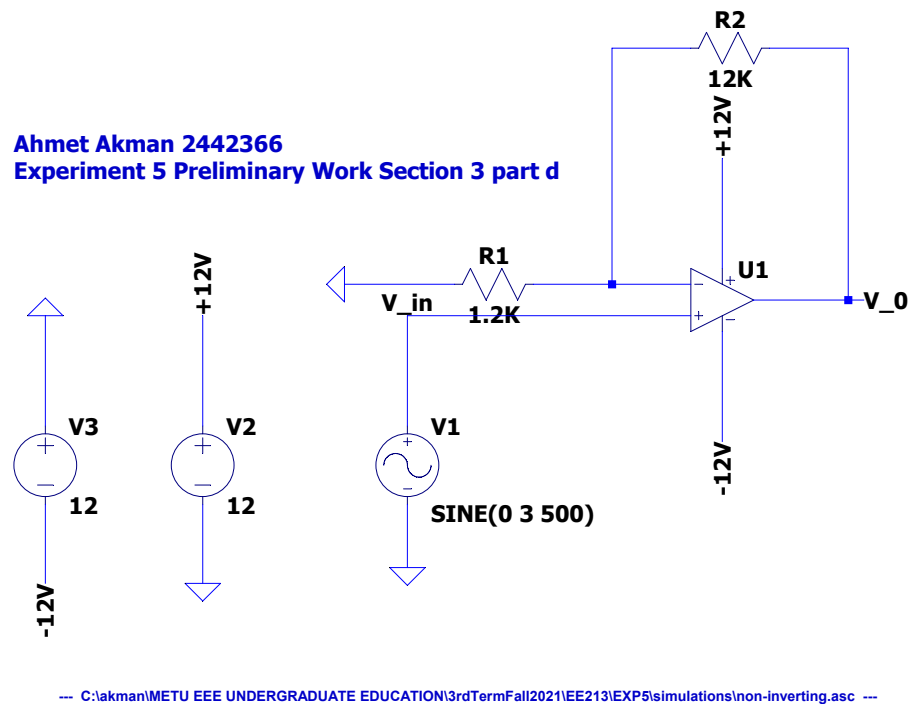


Figure 13: Circuit schematic for the basic comparator.

Then plots given in Figures 17,18 and 19 are obtained.

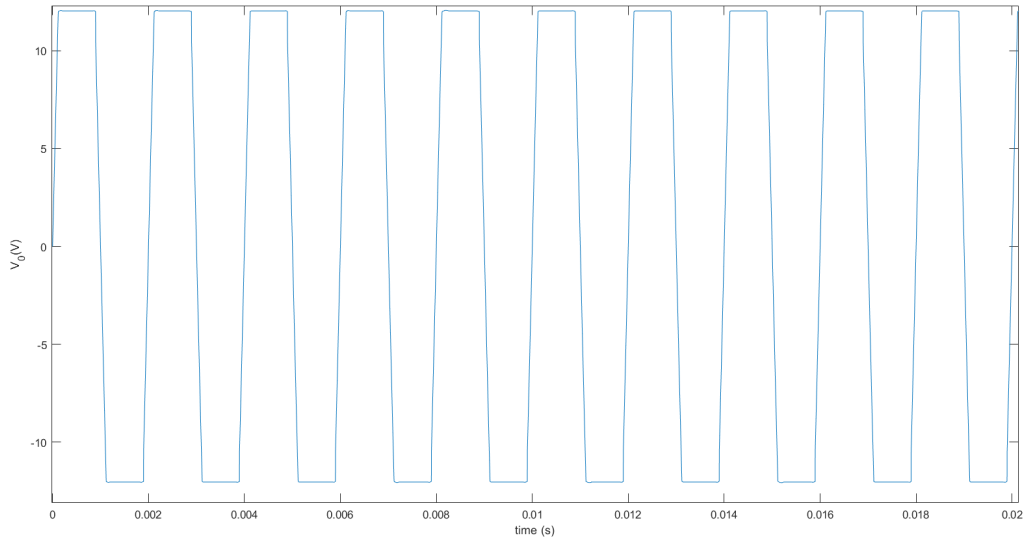


Figure 14: V_0 vs t

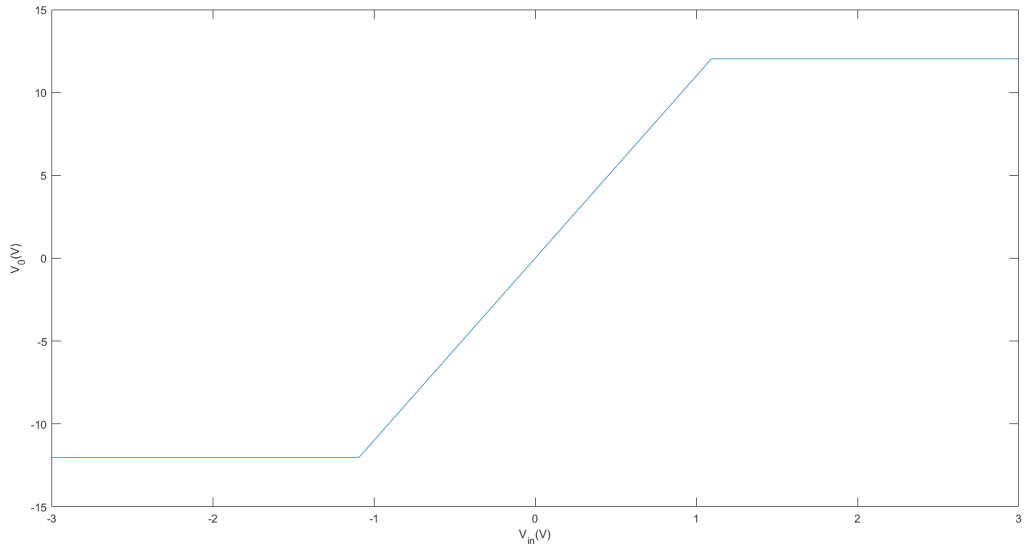


Figure 15: V_0 vs V_{in}

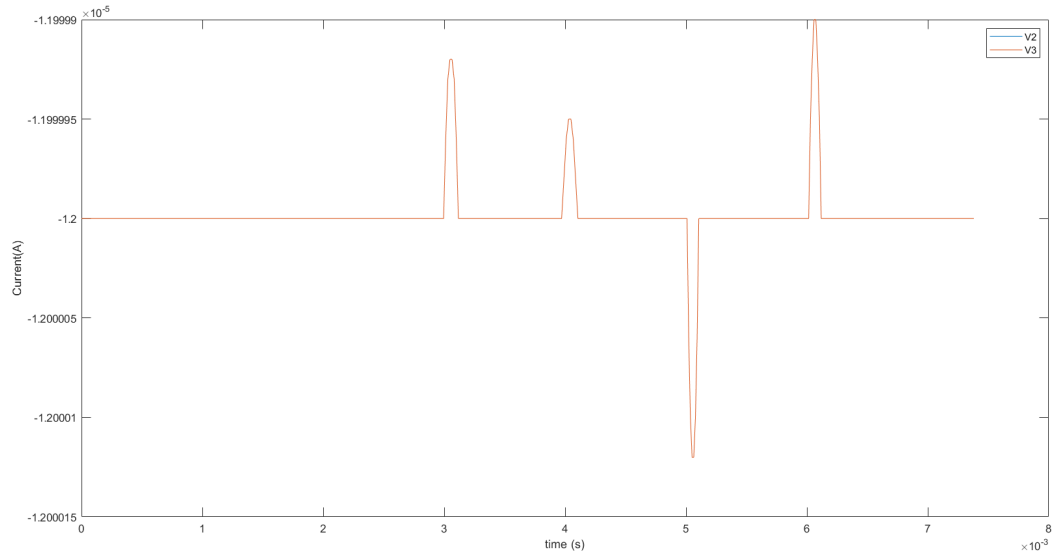


Figure 16: i vs t

5 Step 4

In this step following 2 op-amp circuits are constructed in the LTSpice environment and simulated. V_a is taken as $4\sin(1000\pi)$ Volts. V_b is taken as $2\sin(1000\pi)$ Volts. Then data are fetched from LTSpice and plotted in MATLAB.

5.1 a)

Summing amplifier circuit is constructed in LTSpice environment. The schematic is given in the Figure 20.

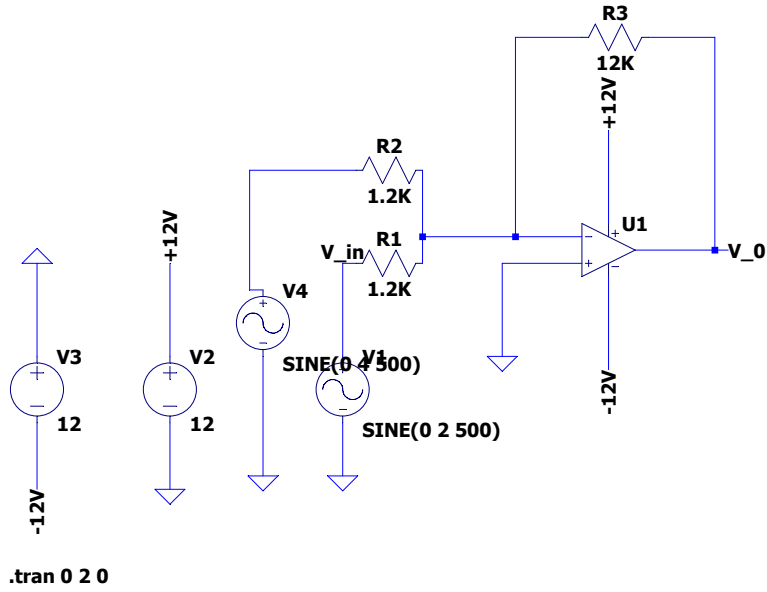


Figure 17: Circuit schematic for the summing amplifier.

Then plots given in Figure 21 is obtained.

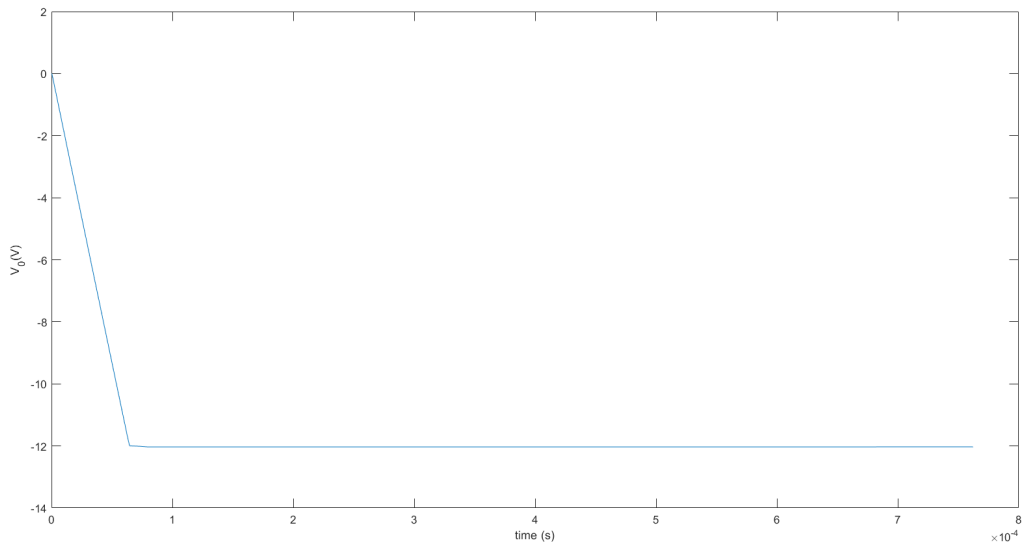


Figure 18: V_0 vs t

5.2 b)

Difference amplifier circuit is constructed in LTSpice environment. The schematic is given in the Figure 22.

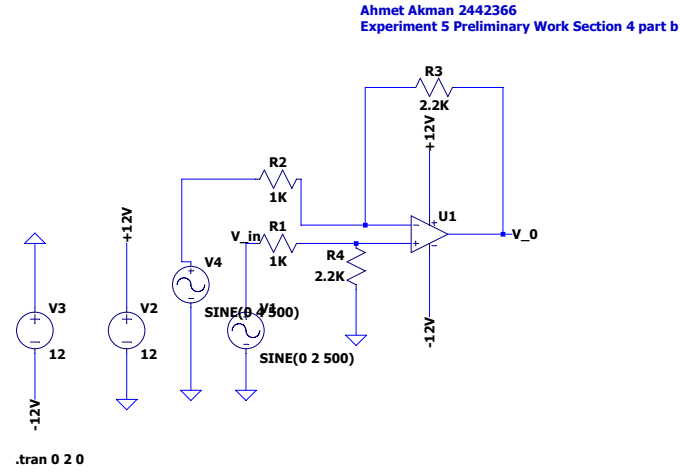


Figure 19: Circuit schematic for the difference amplifier.

Then plots given in Figure 23 is obtained.

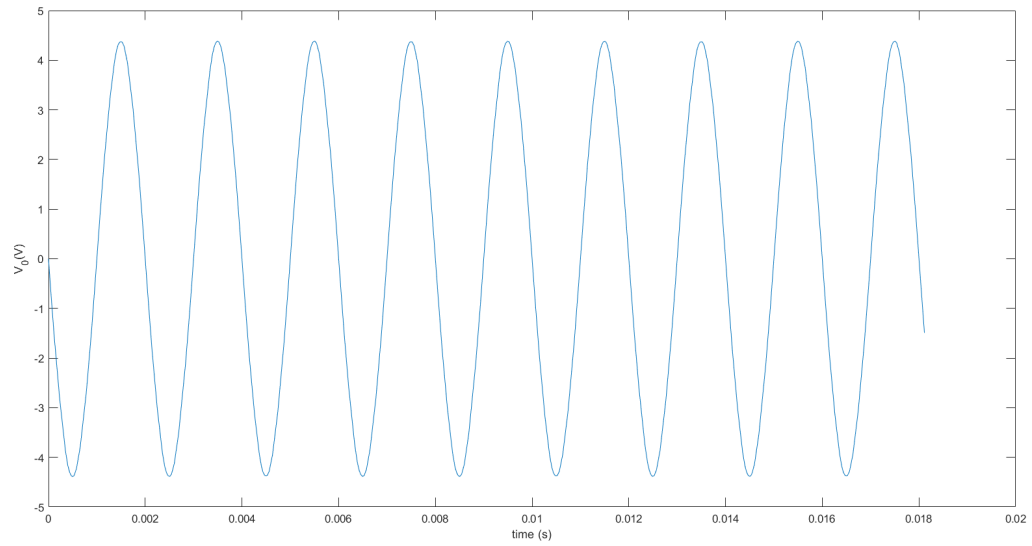


Figure 20: V_0 vs t

6 Step 5

To obtain the expression relating the output voltage $V_o(t)$ to the input voltage $V_{in}(t)$ of a inverting amplifier setup, the circuit in Figure 8 is taken as the reference. Then current through input terminals and the voltage of those terminals are taken as 0 since it is ideal amplifier. So the circuit simplifies to 2 terminals and 2 resistors. Then the following simplifications are followed.

$$\frac{V_{in} - 0}{R_1} = i$$
$$\frac{0 - V_o}{R_2} = i$$

So, the relation becomes as,

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Therefore it seems the plot given in Figure 5 approximately corresponds our findings.

7 Conclusion

In conclusion, in preliminary work of experiment 5, "Operational Amplifiers" needed simulation are made and necessary data are plotted. Then the expression for the inverting amplifier obtained and compared.