

Experiment 4

Resistive Circuits

Ahmet Akman 2442366

Assistant : Şirin Yazar

November 24, 2021

1 Introduction

In this experiment, as students, we are expected to experiment with different kinds of resistive circuits by completing the steps described in the fourth experiment laboratory manual. Throughout these steps, ground loops and output resistances of the signal are expected to be learned. As students, we are expected to discriminate the analog and digital multimeters by considering their internal resistances. The i versus v characteristics is observed by connecting the signal generator to the oscilloscope and the circuit. The nonlinear resistance behavior and how to determine the unknown resistance via Wheatstone Bridge are observed. The results of the steps were recorded and plotted for further comments.

2 Experimental Results

In this section, the results of Experiment 4 are discussed.

2.1 Step 1

2.1.1 a

In this step, the power supply, signal generator, and oscilloscope instruments are used. The circuit given in Figure 1 is constructed. The V_{pp} is selected as 12, and the frequency is adjusted as 50 Hz. Channel 2 of the oscilloscope is connected to the terminals of the rightmost resistor.

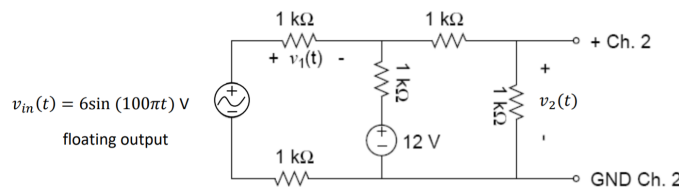


Figure 1: Circuit schematic for the step 1 section *a*

As a result the $V_2(t)$ is observed and plotted. The plotting is given in the Figure 2.

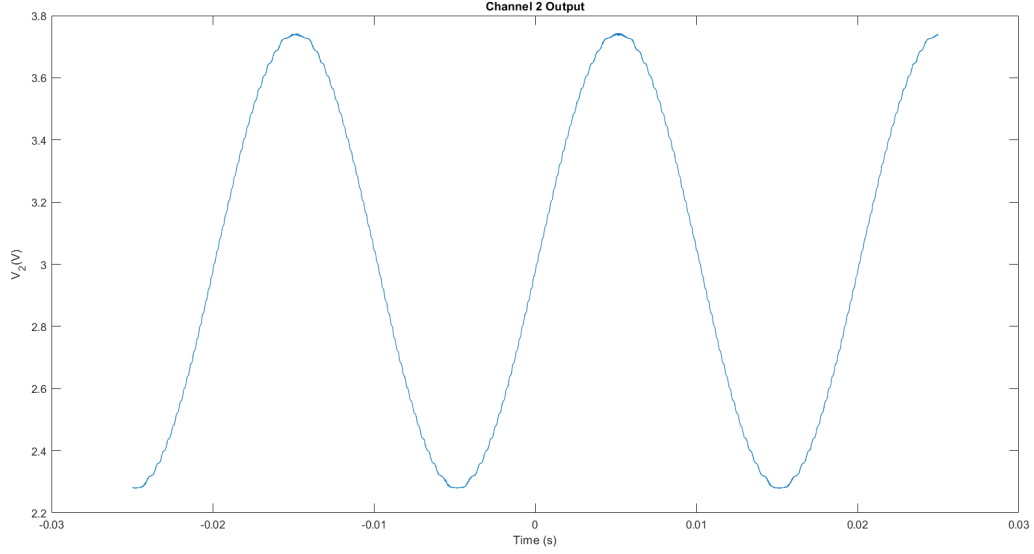


Figure 2: V_2 versus time(s)

2.1.2 b

In this step, the circuit given in Figure 1 is used. As measurement setup, probes of channel 1 are connected additionally. The setup is given in Figure 3.

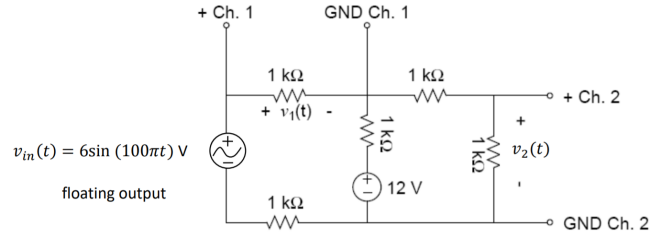


Figure 3: Circuit schematic for the step 1 section b

As a result the values of V_1 and V_2 are observed and plotted. The plotting is given in Figure 4.

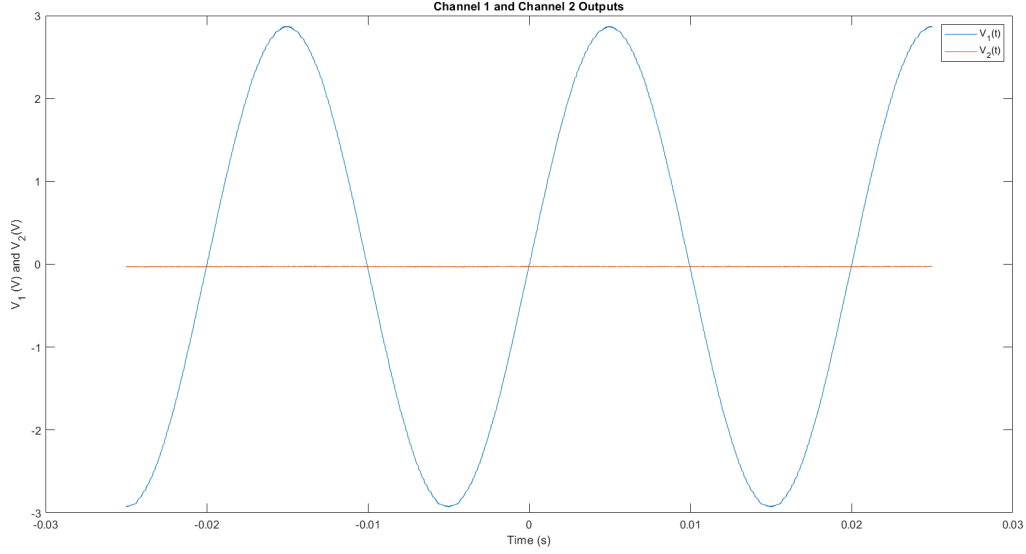


Figure 4: V_1 V_2 versus time(s)

As it can be seen from the plot, channel 2 approximately corresponds to "0" value, although it is not supposed to be so. The measurement probe of the second channel is connected between two ground terminals of the oscilloscope. This result demonstrates that the grounding configuration of the oscilloscope may prevent accurate observations. For comparison, the values measured and calculated theoretically are given in Table 1.

Table 1: Calculated values and measured values.

X	Calculated (V)	Measured (V)
V_1	$\frac{9}{5} \sin 100\pi t - 3$	1.5275
V_2	$\frac{3}{4} \sin 100\pi t + 3$	7.477

Even though the measured values seemed to be accurate and well set during the experiment, it can be inferred that there could be some probing error.

2.2 Step 2

In Step 2, the circuit diagram given in Figure 5 is constructed in the LTspice environment. Measurement probe nodes are indicated with texts on the figure.

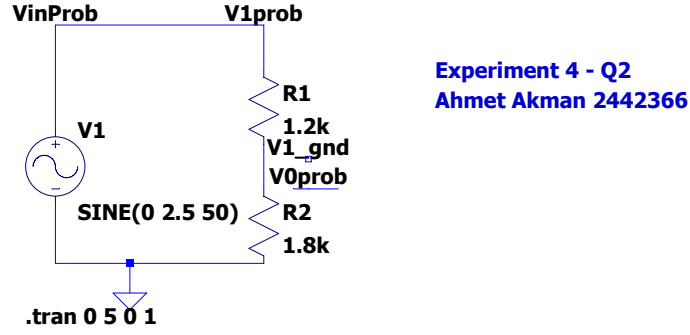


Figure 5: The circuit diagram for the Step 2

2.2.1 a

For the drawn circuit, V_{in} is set as 50 Hz and 5 V_{pp} . As a result the plot given in Figure 6 is obtained.

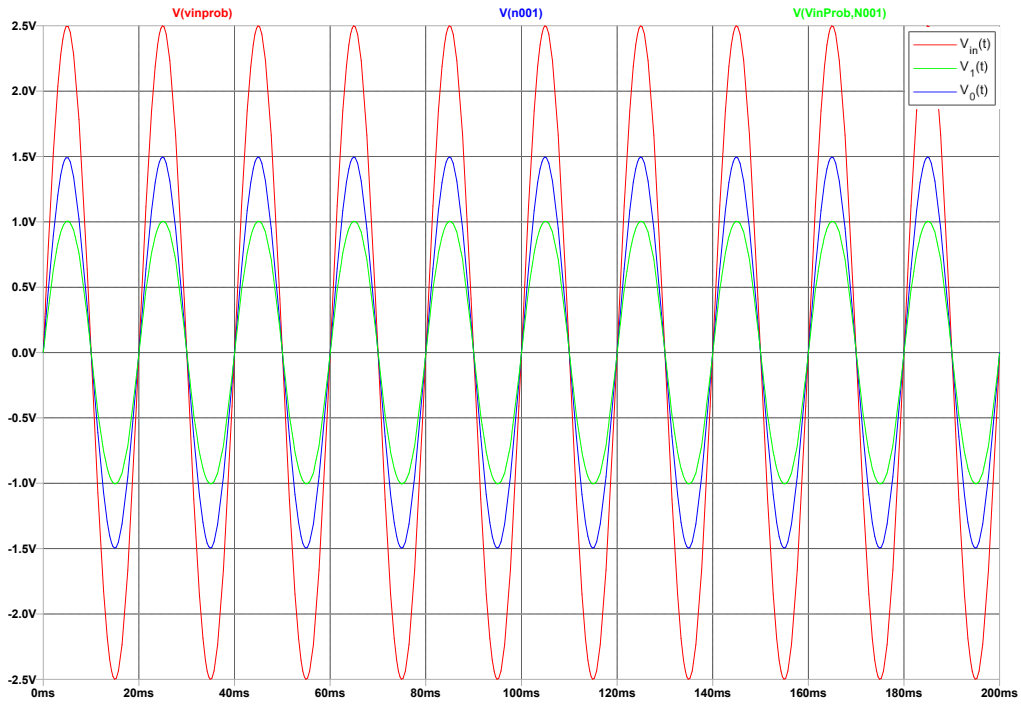


Figure 6: The plot of V_{in} V_0 V_1 versus time(ms)

2.2.2 b

When the V_{in} is displayed only it can be said that V_{pp} is equal to "2" volts which is the same amplitude we found in part a.

2.3 Step 3

In this step, signal generator and oscilloscope instruments are used. The circuit given in the Figure 7 is constructed.

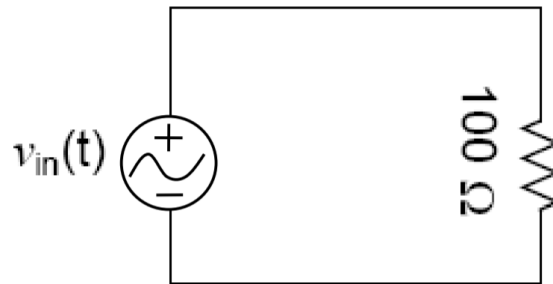


Figure 7: V_{in} versus time (s)

Before connecting the signal generator to the circuit, the terminals are directly connected to the oscilloscope probes. Then the observations are made, and the output is given in Figure 8. The V_{pp} is measured as 3 volts.

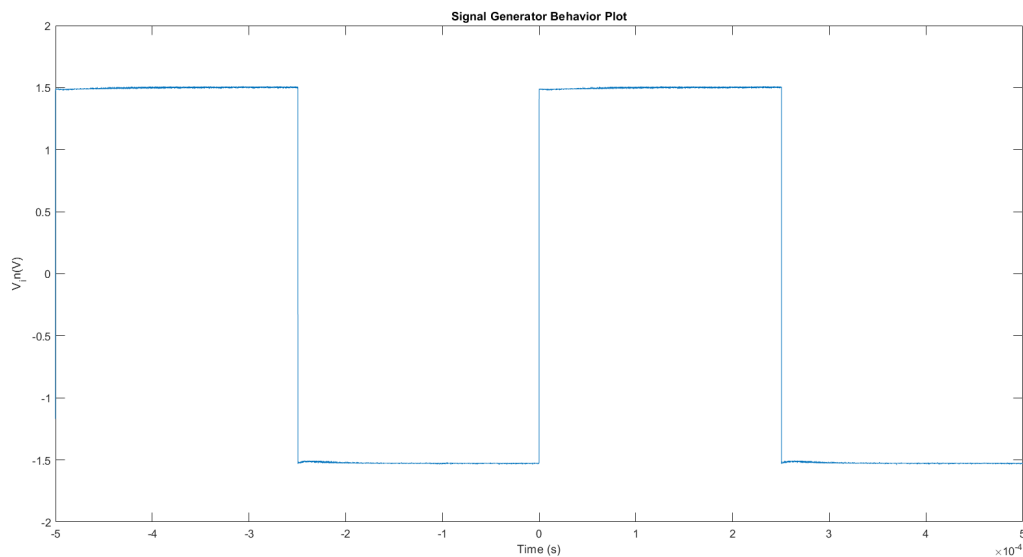


Figure 8: V_{in} versus time (s)

The signal generator is connected to the circuit. The measurements are displayed on the screen of DSO. Then the data plotted are given in Figure 9.

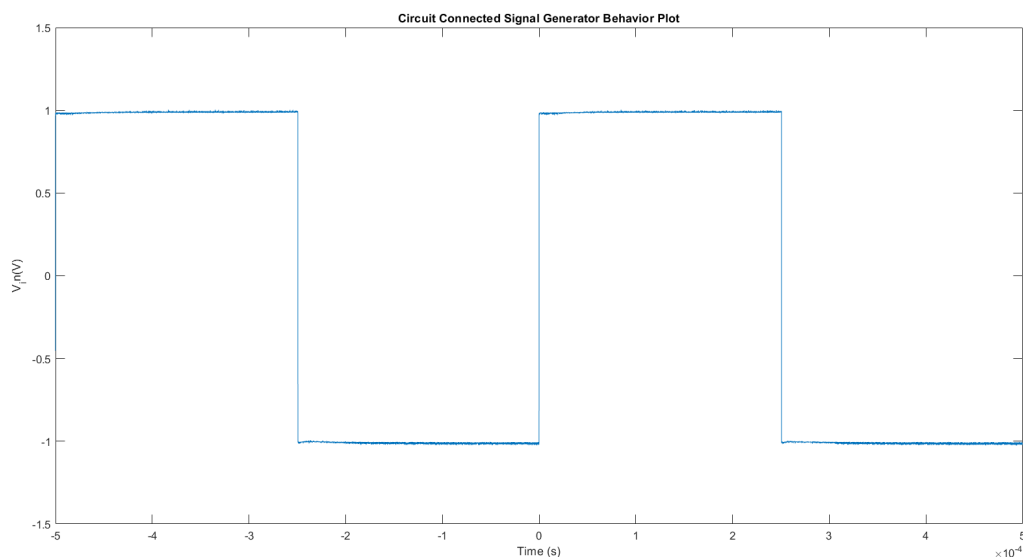


Figure 9: V_{in} versus time (s)

As a result, it can be seen that the drops in the amplitude are stemmed from the non-ideal behavior of the signal generator. It is said that the signal generator has a $50\ \Omega$ internal resistance, so when a comparable resistance is connected, the voltage is divided. It can be seen from Figure 9; the amplitude is dropped to 2 volts.

2.4 Step 4

In this step, the circuits given in the Figure 10 are set. And the source voltage is measured as 5 volts.

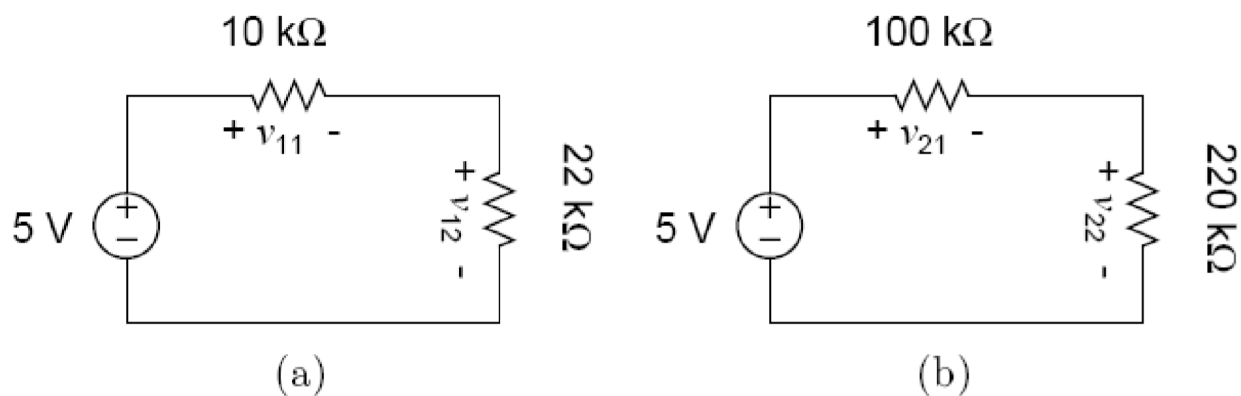


Figure 10: The circuit diagrams for the Step 4

2.4.1 a

The range of the analog multimeter is set to 5 V DC. The internal resistance of the analog multimeter is measured via digital multimeters resistance mode. The obtained internal resistance is "99.705k Ω ". All the voltage measurements are made using analog multimeter.

2.4.2 b

All the measurements are repeated and recorded using digital multimeter. For the comparison, the readings of the analog and digital multimeters are given in the Table 2.

Table 2: Analog and digital measurements

X	Analog Reading (V)	Digital Reading (V)
V_{11}	1.4	1.594
V_{12}	3.1	3.406
V_{21}	0.87	1.539
V_{22}	1.95	3.430

There are two results that can be inferred. Firstly, the analog multimeters measurements are quite inconsistent, especially for the second circuit. This can be stemmed from the fact that the internal resistance of the analog multimeter is measured as a comparable value to the equivalent resistance of the second circuit. Secondly, the digital multimeter measures more accurate than the analog multimeter. The reason is that the digital multimeter can adjust its internal resistance so that the measurements are made properly.

2.5 Step 5

2.5.1 a

In Step 2, the circuit diagram given in the Figure 11 is constructed in the LTspice environment.

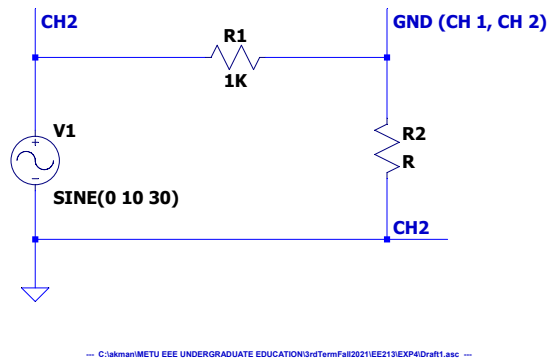


Figure 11: The LTspice diagram for Step 5 part a

The resistance values are selected as 1K , 5K and 10K. Then the simulation is run, the data is fetched from the LTspice and plotted at the MATLAB. The plot can be seen from the Figure 12.

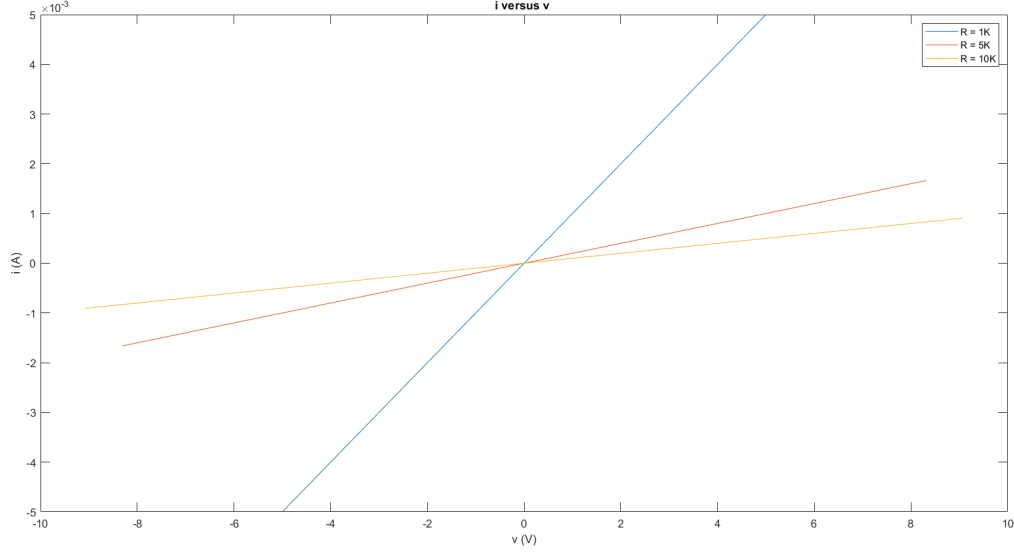


Figure 12: i versus v plot

We can obtain the resistance values from the slope of the i-v lines. We can get the current through unknown R via directly CH2 measurement. We had to invert the CH1 to get i versus v characteristic in XY mode.

2.5.2 b

In the part b, the circuit diagram given in the Figure 13 is constructed in the LTspice environment.

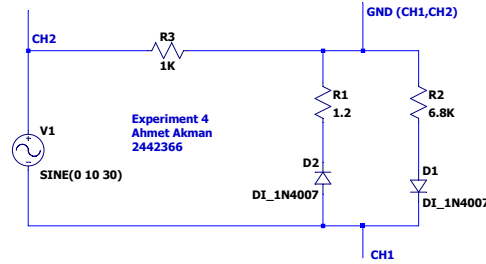


Figure 13: The LTspice diagram for Step 5 part b

The simulation is rerun, the data is fetched from the LTspice and plotted at the MATLAB. The plot can be seen from the Figure 14.

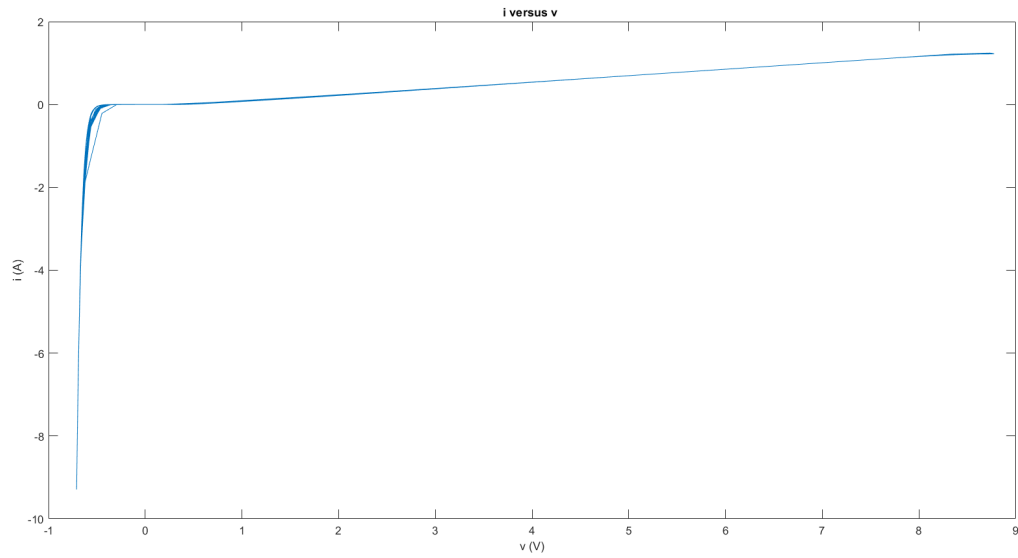


Figure 14: i versus v plot

We can conclude from the plot that the equivalent resistance changes when the voltage direction change. The nonideal behavior is stemmed from the 0.7 V tolerance of the diodes.

2.6 Step 6

In this step the Wheatstone Bridge circuit in the Figure 15 is set.

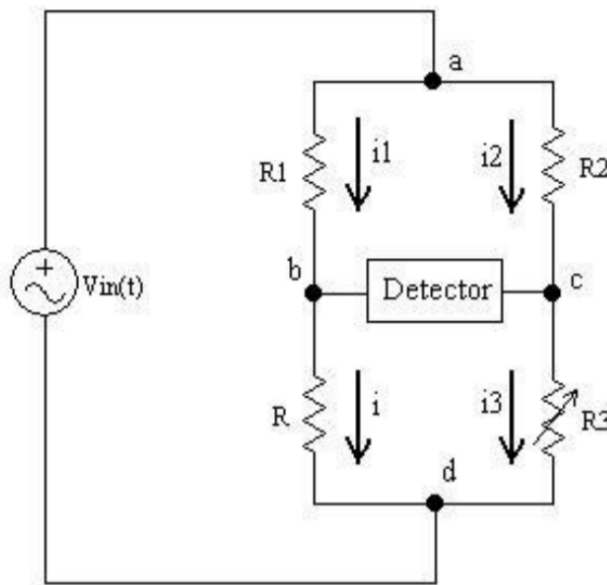


Figure 15: Circuit diagram for Step 6

For R1 and R2 $1.2\text{K}\Omega$ resistors are used. For R3 $6.8\text{k}\Omega$ resistor is used. Then $10\text{k}\Omega$ pot is properly adjusted so that the voltage between nodes b and c equals 0. To learn the value of R3, the potentiometer is unplugged from the breadboard, and its resistance is measured as " $6.907\text{k}\Omega$ ".

3 Conclusion

In conclusion, in experiment 4, "Resistive Circuits," as students, we have learned how the resistive elements and some laboratory equipment behave in general. The experiment was conducted in 6 steps. Firstly, the grounding setup of the oscilloscope is observed on a resistive circuit with two sources. Then LTspice simulations are made and observed for 2 resistors in the series circuit. Then the nonideal behavior of the signal generator due to its internal resistance has experimented. Also, the internal resistance effect to the analog multimeter is observed, and its accuracy is compared to the digital multimeter. I versus v characteristics are observed on simulations of different set circuits. Lastly, we have learned how to determine the value of an unknown resistor using the Wheatstone Bridge circuit. In this experiment, as students, we have experimented with different characteristics of resistive circuits and laboratory instruments and we have learned how to work with an LTspice simulation environment.

Appendix I

Total time spent on/during:

- Pre-lab preparation: 2 hours (including the preliminary work and simulations)
- Experimental work: 2 hours (hours spent in lab)
- Report writing: 8 hours